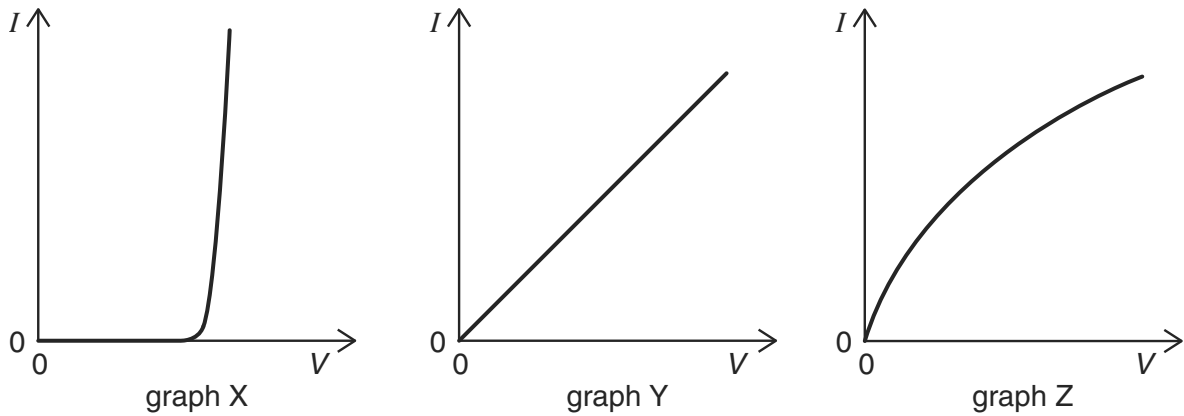


- 1 The graphs show the variation with potential difference  $V$  of the current  $I$  for three circuit elements.

9702/1/M/J/02




The three circuit elements are a metal wire at constant temperature, a semiconductor diode and a filament lamp.

Which row of the table correctly identifies these graphs?

	metal wire at constant temperature	semiconductor diode	filament lamp
<b>A</b>	X	Z	Y
<b>B</b>	Y	X	Z
<b>C</b>	Y	Z	X
<b>D</b>	Z	X	Y

- 2 The graph shows how the current through a lamp filament varies with the potential difference across it.

9702/1/O/N/02

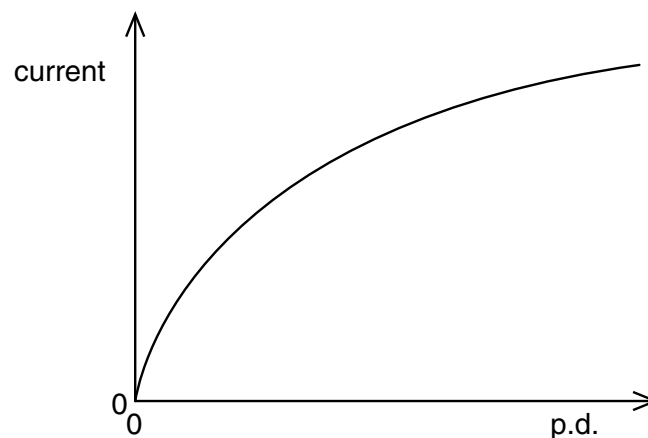

Which statement explains the shape of this graph?

- A** As the filament temperature rises, electrons can pass more easily through the filament.
- B** It takes time for the filament to reach its working temperature.
- C** The power output of the filament is proportional to the square of the current through it.
- D** The resistance of the filament increases with a rise in temperature.

- 3 The filament of a 240 V, 100 W electric lamp heats up from room temperature to its operating temperature. As it heats up, its resistance increases by a factor of 16.


9702/1/M/J/02

What is the resistance of this lamp at room temperature?

- A** 36  $\Omega$       **B** 580  $\Omega$       **C** 1.5 k $\Omega$       **D** 9.2 k $\Omega$

- 4 The variation with potential difference  $V$  of the current  $I$  in a semiconductor diode is shown below.

9702/1/O/N/02

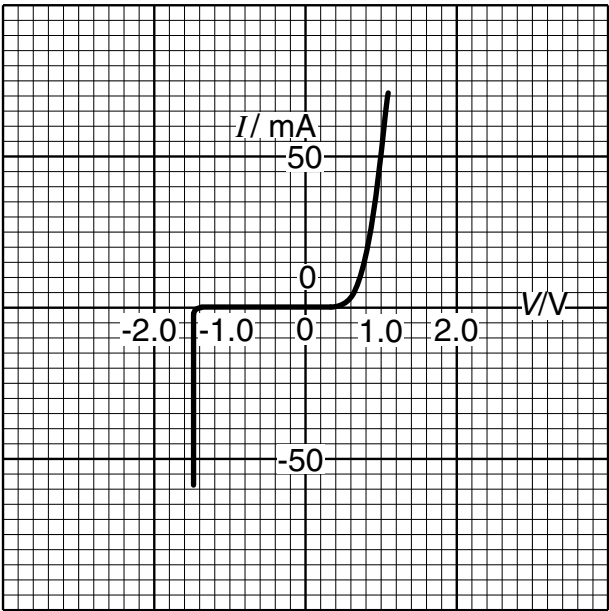

What is the resistance of the diode for applied potential differences of +1.0 V and –1.0 V?

	resistance	
	at +1.0 V	at –1.0 V
<b>A</b>	20 $\Omega$	infinite
<b>B</b>	20 $\Omega$	zero
<b>C</b>	0.05 $\Omega$	infinite
<b>D</b>	0.05 $\Omega$	zero

- 5 Two wires made of the same material and of the same length are connected in parallel to the same voltage supply. Wire P has a diameter of 2 mm. Wire Q has a diameter of 1 mm.


9702/01/M/J/04

What is the ratio  $\frac{\text{current in P}}{\text{current in Q}}$  ?

- A**  $\frac{1}{4}$       **B**  $\frac{1}{2}$       **C** 2      **D** 4

- 6 Which diagram shows a potential divider circuit that can vary the voltage across the lamp?

9702/01/O/N/03

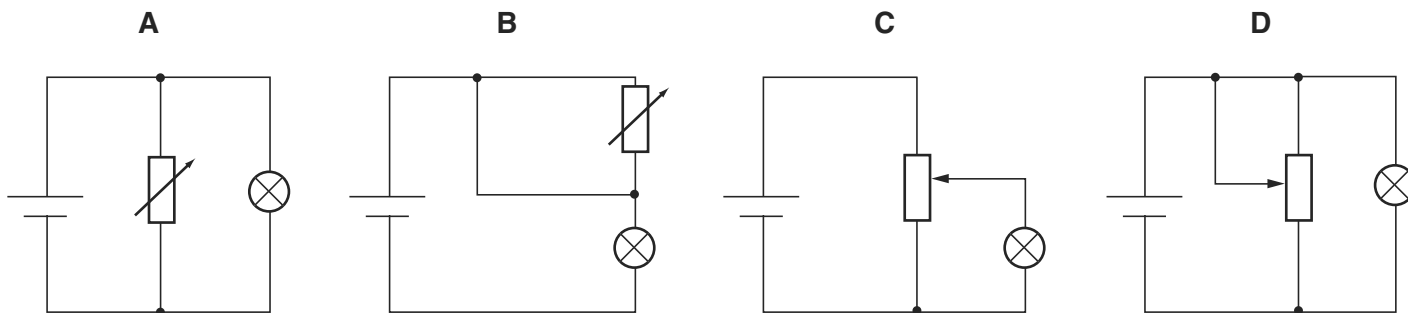

- 7 When a potential difference  $V$  is applied between the ends of a wire of diameter  $d$  and length  $l$ , the current in the wire is  $I$ .

9702/01/O/N/04

What is the current when a potential difference of  $2V$  is applied between the ends of a wire of the same material of diameter  $2d$  and the length  $2l$ ? Assume that the temperature of the wire remains constant.


- A  $I$                       B  $2I$                       C  $4I$                       D  $8I$
- 8 A cylindrical piece of a soft, electrically-conducting material has resistance  $R$ . It is rolled out so that its length is doubled but its volume stays constant.

9702/01/M/J/05

What is its new resistance?

- A  $\frac{R}{2}$                       B  $R$                       C  $2R$                       D  $4R$
- 9 The  $I$ - $V$  characteristics of two electrical components P and Q are shown below.

9702/01/M/J/05

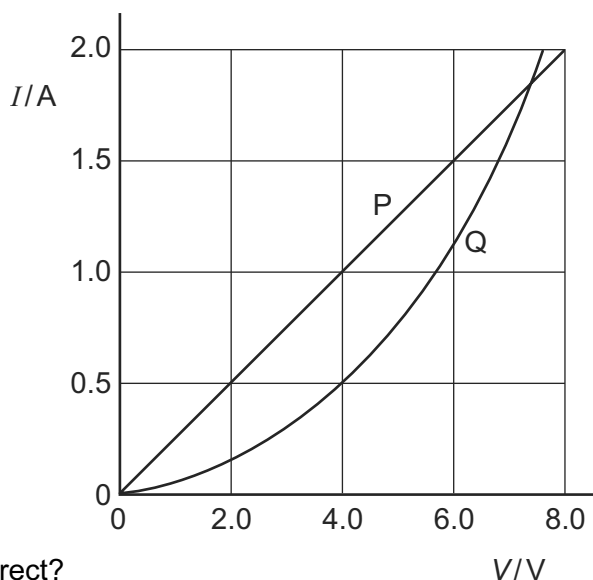


Which statement is correct?

- A P is a resistor and Q is a filament lamp.
- B The resistance of Q increases as the current in it increases.
- C At  $1.9\text{ A}$  the resistance of Q is approximately half that of P.
- D At  $0.5\text{ A}$  the power dissipated in Q is double that in P.

- 10 Tensile strain may be measured by the change in electrical resistance of a strain gauge. A strain gauge consists of folded fine metal wire mounted on a flexible insulating backing sheet. The strain gauge is firmly attached to the specimen, so that the strain in the metal wire is always identical to that in the specimen.

9702/01/O/N/05

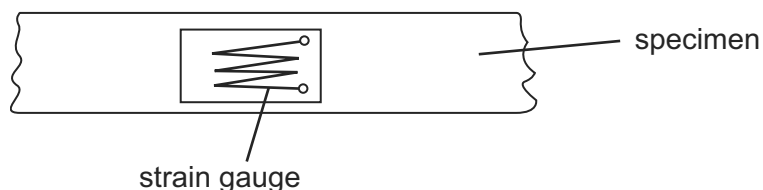


When the strain in the specimen is increased, what happens to the resistance of the wire?

- A** It decreases, because the length decreases and the cross-sectional area increases.  
**B** It decreases, because the length increases and the cross-sectional area decreases.  
**C** It increases, because the length decreases and the cross-sectional area increases.  
**D** It increases, because the length increases and the cross-sectional area decreases.
- 11 A metal wire of length 0.50 m has a resistance of  $12\ \Omega$ .
- What is the resistance of a wire of length 2.0 m and made of the same material, but with half the diameter?
- A**  $12\ \Omega$       **B**  $48\ \Omega$       **C**  $96\ \Omega$       **D**  $192\ \Omega$
- 12 The graph shows how the electric current  $I$  through a conducting liquid varies with the potential difference  $V$  across it.


9702/01/O/N/05

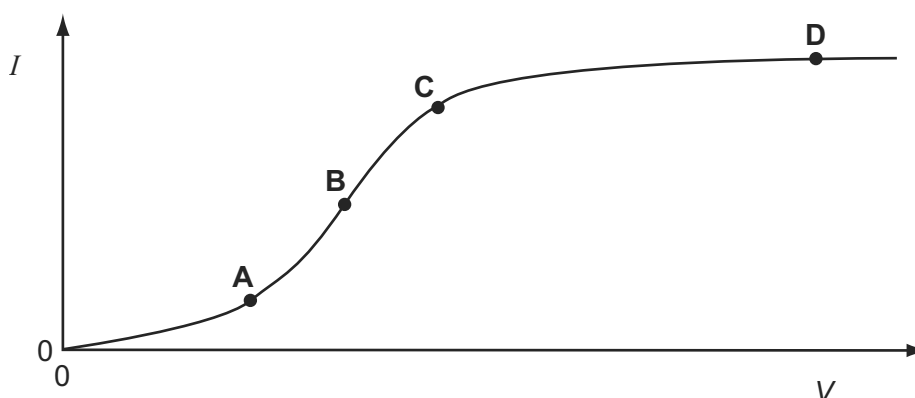At which point on the graph does the liquid have the smallest resistance?




- 13 Which graph shows the  $I - V$  characteristic of a filament lamp?

9702/01/O/N/06

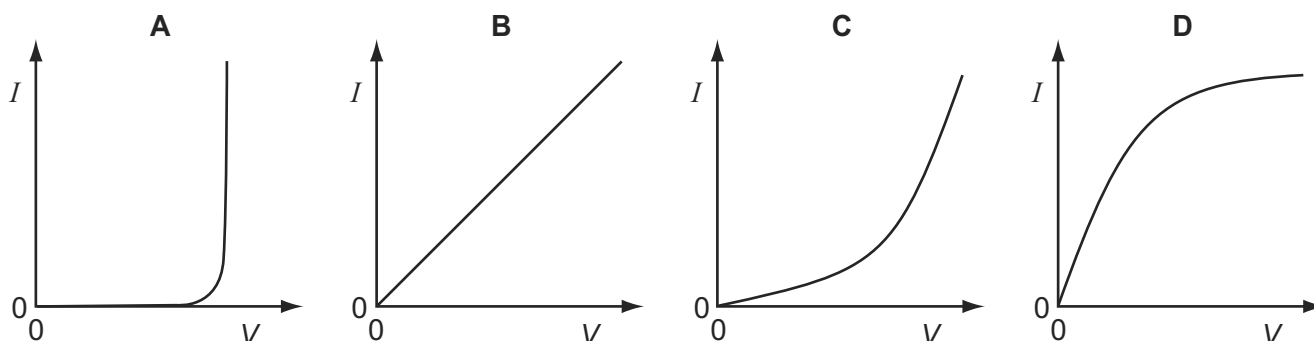

- 14 An electrical component has a potential difference  $V$  across it and a current  $I$  through it. A graph of  $I$  against  $V$  is drawn and is marked in three sections WX, XY and YZ.

9702/01/O/N/06

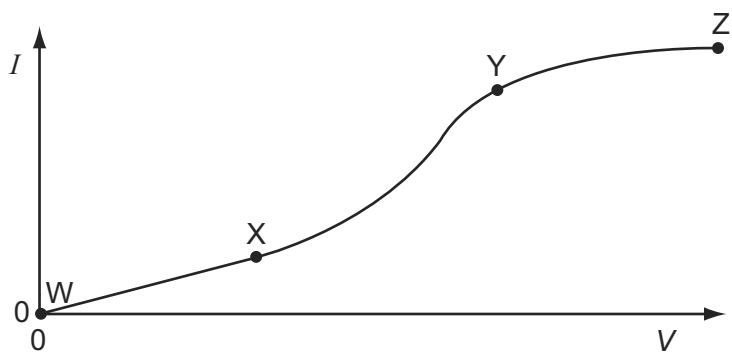


In which ways does the resistance of the component vary within each of the three sections?


	WX	XY	YZ
<b>A</b>	constant	decreases	increases
<b>B</b>	constant	increases	increases
<b>C</b>	increases	decreases	constant
<b>D</b>	increases	increases	decreases

- 15 A researcher has two pieces of copper of the same volume. All of the first piece is made into a cylindrical resistor P of length  $x$ .

9702/01/M/J/07

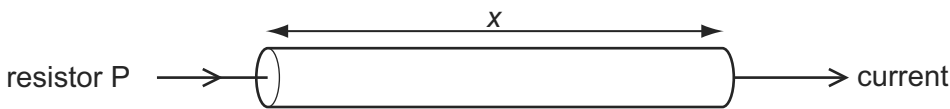

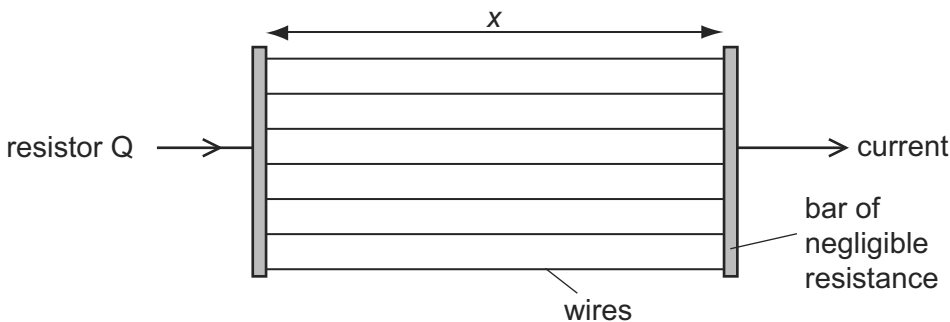All of the second piece is made into uniform wires each of the same length  $x$  which he connects between two bars of negligible resistance to form a resistor Q.



How do the electrical resistances of P and Q compare?


- A** P has a larger resistance than Q.
- B** Q has a larger resistance than P.
- C** P and Q have equal resistance.
- D** Q may have a larger or smaller resistance than P, depending on the number of wires made.

- 16 Two wires P and Q have resistances  $R_P$  and  $R_Q$  respectively. Wire P is twice as long as wire Q and has twice the diameter of wire Q. The wires are made of the same material. 9702/01/O/N/07

What is the ratio  $\frac{R_P}{R_Q}$ ?

- A 0.5                      B 1                      C 2                      D 4

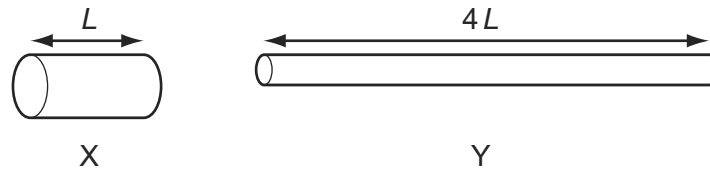- 17 Two copper wires X and Y have the same volume. Wire Y is four times as long as wire X. 9702/01/M/J/08



What is the ratio  $\frac{\text{resistance of wire Y}}{\text{resistance of wire X}}$ ?


- A 4                      B 8                      C 16                      D 64

- 18 Two wires P and Q made of the same material and of the same length are connected in parallel to the same voltage supply. Wire P has diameter 2 mm and wire Q has diameter 1 mm. 9702/01/O/N/08

What is the ratio  $\frac{\text{current in P}}{\text{current in Q}}$ ?

- A  $\frac{1}{4}$                       B  $\frac{1}{2}$                       C  $\frac{2}{1}$                       D  $\frac{4}{1}$

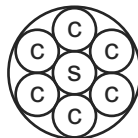- 19 An electric power cable consists of six copper wires c surrounding a steel core s. 9702/01/O/N/08



1.0 km of one of the copper wires has a resistance of  $10\ \Omega$  and 1.0 km of the steel core has a resistance of  $100\ \Omega$ .

What is the approximate resistance of a 1.0 km length of the power cable?

- A  $0.61\ \Omega$                       B  $1.6\ \Omega$                       C  $160\ \Omega$                       D  $610\ \Omega$

- 20 A copper wire is cylindrical and has resistance  $R$ . 9702/11/O/N/10

What will be the resistance of a copper wire of twice the length and twice the radius?

- A  $\frac{R}{4}$                       B  $\frac{R}{2}$                       C  $R$                       D  $2R$

- 21 What is the unit of resistivity? 9702/11/M/J/10

- A  $\Omega\text{m}^{-2}$                       B  $\Omega\text{m}^{-1}$                       C  $\Omega$                       D  $\Omega\text{m}$

- 22** A cylindrical wire 4.0 m long has a resistance of  $31\ \Omega$  and is made of metal of resistivity  $1.0 \times 10^{-6}\ \Omega\text{m}$ .  
9702/11/O/N/09

What is the radius of cross-section of the wire?

- A**  $1.0 \times 10^{-8}\text{ m}$
- B**  $2.0 \times 10^{-8}\text{ m}$
- C**  $6.4 \times 10^{-8}\text{ m}$
- D**  $2.0 \times 10^{-4}\text{ m}$

- 23** A power cable has length 2000 m. The cable is made of twelve parallel strands of copper wire, each with diameter 0.51 mm.  
9702/12/M/J/13

What is the resistance of the cable? (resistivity of copper =  $1.7 \times 10^{-8}\ \Omega\text{m}$ )

- A**  $0.014\ \Omega$       **B**  $3.5\ \Omega$       **C**  $14\ \Omega$       **D**  $166\ \Omega$


- 24** A copper wire is to be replaced by an aluminium alloy wire of the same length and resistance. Copper has half the resistivity of the alloy.  
9702/12/M/J/14

What is the ratio  $\frac{\text{diameter of alloy wire}}{\text{diameter of copper wire}}$ ?

- A**  $\sqrt{2}$       **B** 2      **C**  $2\sqrt{2}$       **D** 4

- 25** When a thin metal wire is stretched, it becomes longer and thinner. This causes a change in the resistance of the wire. The volume of the wire remains constant.  
9702/12/M/J/15

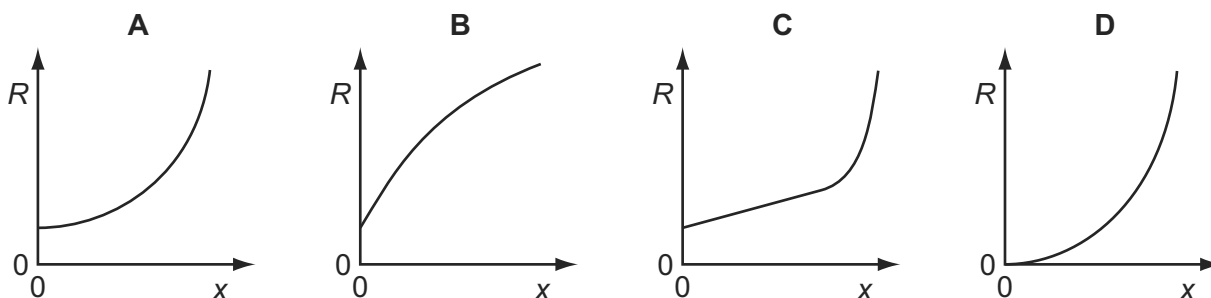Which graph could represent the variation with extension  $x$  of the resistance  $R$  of the wire?




- 26** A pencil is used to draw a line of length 30 cm and width 1.2 mm. The resistivity of the material in the pencil is  $2.0 \times 10^{-5}\ \Omega\text{m}$  and the resistance of the line is  $40\ \text{k}\Omega$ .  
9702/11/O/N/14

What is the thickness of the line?

- A**  $1.25 \times 10^{-10}\text{ m}$
- B**  $1.25 \times 10^{-8}\text{ m}$
- C**  $1.25 \times 10^{-7}\text{ m}$
- D**  $1.25 \times 10^{-5}\text{ m}$





- 27** A conductor consists of three wires connected in series. The wires are all made of the same metal but have different cross-sectional areas. There is a current  $I$  in the conductor.

9702/11/O/N/14

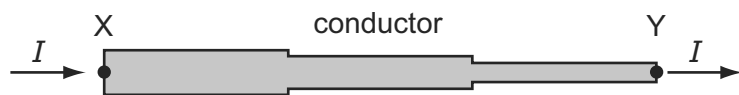

Point Y on the conductor is at zero potential.

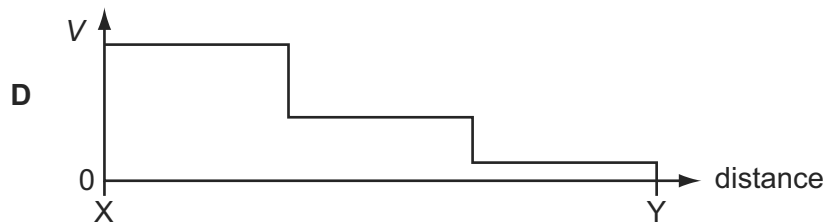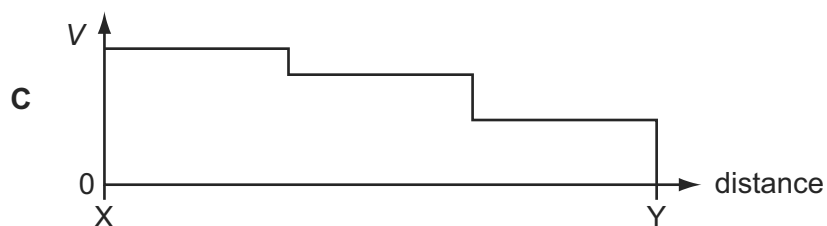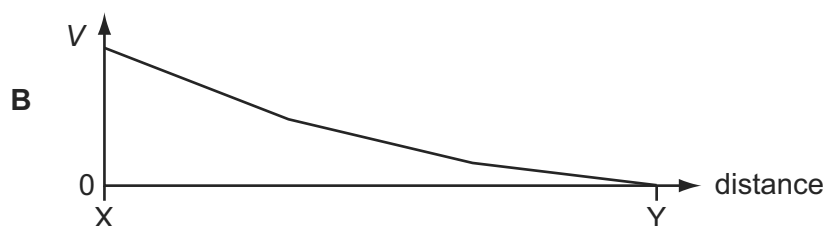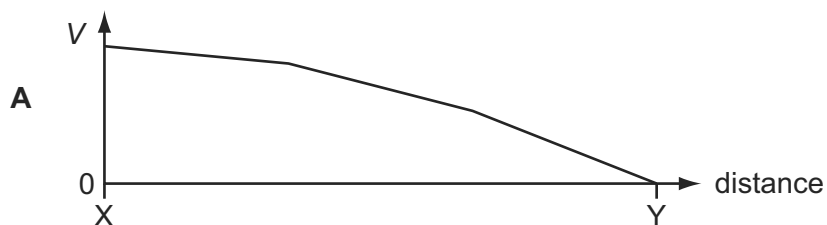
Which graph best shows the variation of potential  $V$  with distance along the conductor?









- 28 A wire PQ is made of three different materials, with resistivities  $\rho$ ,  $2\rho$  and  $3\rho$ . There is a current  $I$  in this composite wire, as shown.

9702/12/O/N/10

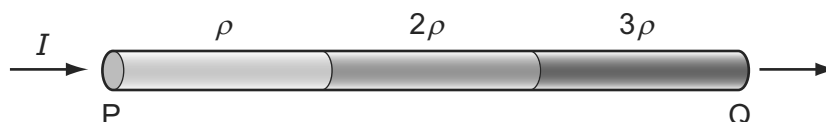

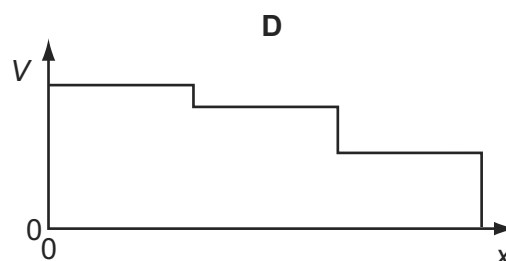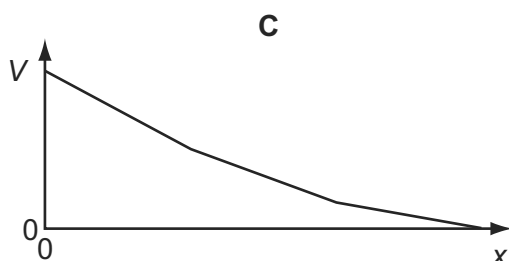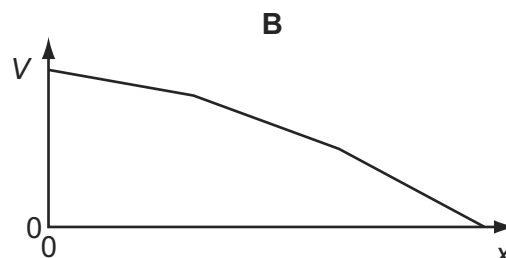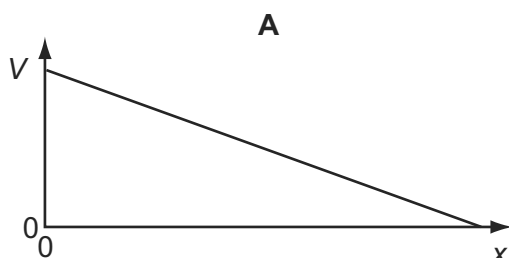Which graph best shows how the potential  $V$  along the wire varies with distance  $x$  from P?



- 29 The wire of a heating element has resistance  $R$ . The wire breaks and is replaced by a different wire.

9702/11/O/N/13


Data for the original wire and the replacement wire are shown in the table.

	length	diameter	resistivity of metal
original wire	$l$	$d$	$\rho$
replacement wire	$l$	$2d$	$2\rho$

What is the resistance of the replacement wire?

- A**  $\frac{R}{4}$       **B**  $\frac{R}{2}$       **C**  $R$       **D**  $2R$

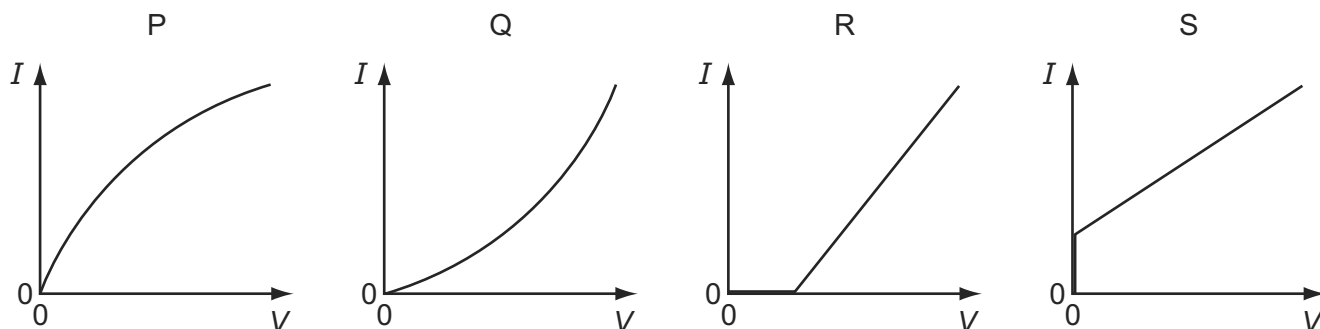
- 30 The graphs show possible current-voltage ( $I$ - $V$ ) relationships for a filament lamp and for a semiconductor diode. 9702/11/M/J/11



Which row best specifies the correct  $I$ - $V$  graphs for the lamp and the diode?

	filament lamp	semiconductor diode
<b>A</b>	P	R
<b>B</b>	P	S
<b>C</b>	Q	R
<b>D</b>	Q	S

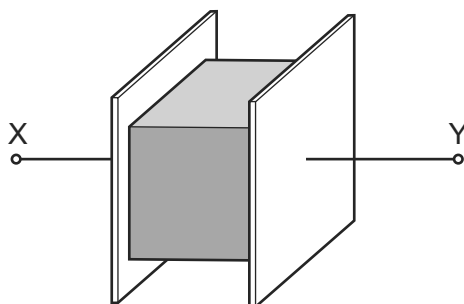- 31 The resistance of a metal cube is measured by placing it between two parallel plates, as shown. 9702/13/M/J/11



The cube has volume  $V$  and is made of a material with resistivity  $\rho$ . The connections to the cube have negligible resistance.

Which expression gives the electrical resistance of the metal cube between X and Y?

- A**  $\rho V^{\frac{1}{3}}$      
 **B**  $\rho V^{\frac{2}{3}}$      
 **C**  $\frac{\rho}{V^{\frac{1}{3}}}$      
 **D**  $\frac{\rho}{V^{\frac{2}{3}}}$

- 32 An iron wire has length 8.0 m and diameter 0.50 mm. The wire has resistance  $R$ . 9702/11/M/J/12

A second iron wire has length 2.0 m and diameter 1.0 mm.


What is the resistance of the second wire?

- A**  $\frac{R}{16}$      
 **B**  $\frac{R}{8}$      
 **C**  $\frac{R}{2}$      
 **D**  $R$

- 33 Two electrically-conducting cylinders X and Y are made from the same material.

9702/12/O/N/11

Their dimensions are as shown.

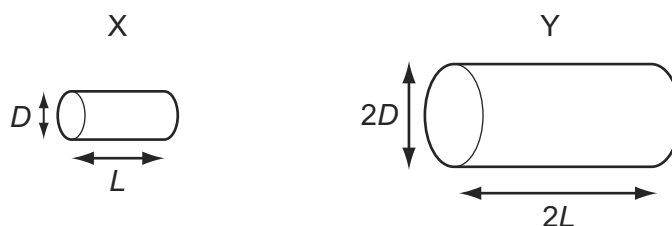


The resistance of each cylinder is measured between its ends.

What is the ratio  $\frac{\text{resistance of X}}{\text{resistance of Y}}$ ?

- A  $\frac{2}{1}$       B  $\frac{1}{1}$       C  $\frac{1}{2}$       D  $\frac{1}{4}$

- 34 The graph shows the variation with potential difference (p.d.) of the current in a lamp filament.

9702/12/O/N/11

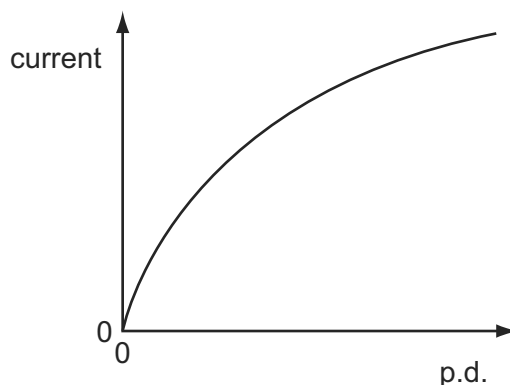

Which statement explains the shape of this graph?

- A As the filament temperature rises, electrons can pass more easily through the filament.  
B It takes time for the filament to reach its working temperature.  
C The power output of the filament is proportional to the square of the current in it.  
D The resistance of the filament increases with a rise in temperature.


- 35 Which statement about electrical resistivity is correct?

9702/11/O/N/11

- A The resistivity of a material is numerically equal to the resistance in ohms of a cube of that material, the cube being of side length one metre and the resistance being measured between opposite faces.  
B The resistivity of a material is numerically equal to the resistance in ohms of a one metre length of wire of that material, the area of cross-section of the wire being one square millimetre and the resistance being measured between the ends of the wire.  
C The resistivity of a material is proportional to the cross-sectional area of the sample of the material used in the measurement.  
D The resistivity of a material is proportional to the length of the sample of the material used in the measurement.

- 36** Two wires P and Q made of the same material are connected to the same electrical supply. P has twice the length of Q and one-third of the diameter of Q, as shown in the diagram.

9702/12/M/J/13

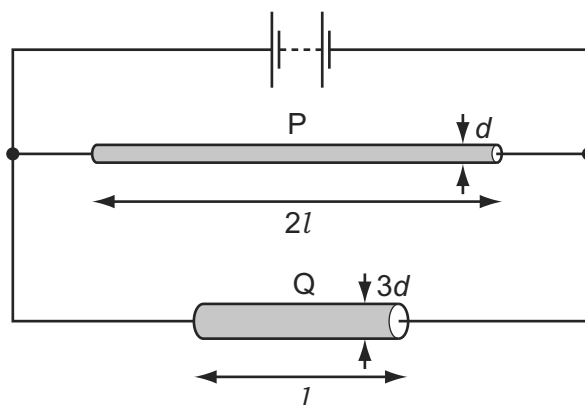

What is the ratio  $\frac{\text{current in P}}{\text{current in Q}}$ ?

- A**  $\frac{2}{3}$       **B**  $\frac{2}{9}$       **C**  $\frac{1}{6}$       **D**  $\frac{1}{18}$

- 36** A cylindrical wire of length 10 m and diameter 2.0 mm has a resistance of  $0.050\ \Omega$ . 9702/11/O/N/12

From which material is the wire made?

	material	resistivity/ $\Omega\text{ m}$
<b>A</b>	bronze	$1.6 \times 10^{-7}$
<b>B</b>	nichrome	$1.6 \times 10^{-6}$
<b>C</b>	silver	$1.6 \times 10^{-8}$
<b>D</b>	zinc	$6.3 \times 10^{-8}$

- 38** A copper wire is stretched so that its diameter is reduced from 1.0 mm to a uniform 0.5 mm.

9702/12/O/N/12


The resistance of the unstretched copper wire is  $0.2\ \Omega$ .

What will be the resistance of the stretched wire?

- A**  $0.4\ \Omega$       **B**  $0.8\ \Omega$       **C**  $1.6\ \Omega$       **D**  $3.2\ \Omega$

- 39 The graph shows the variation with length  $l$  of resistance  $R$  for two wires X and Y made from the same material.


9702/12/O/N/12

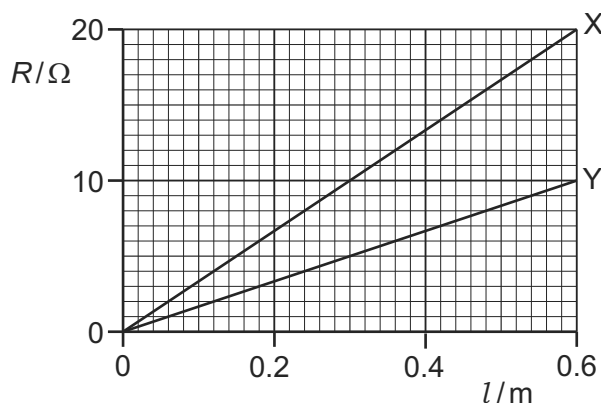

What does the graph show?

- A cross-sectional area of X =  $2 \times$  cross-sectional area of Y
  - B resistivity of X =  $2 \times$  resistivity of Y
  - C when equal lengths of X and Y are connected in series to a battery, power in X =  $2 \times$  power in Y
  - D when equal lengths of X and Y are connected in parallel to a battery, current in X =  $2 \times$  current in Y
- 40 The graph shows how current  $I$  varies with voltage  $V$  for a filament lamp.

9702/13/M/J/13

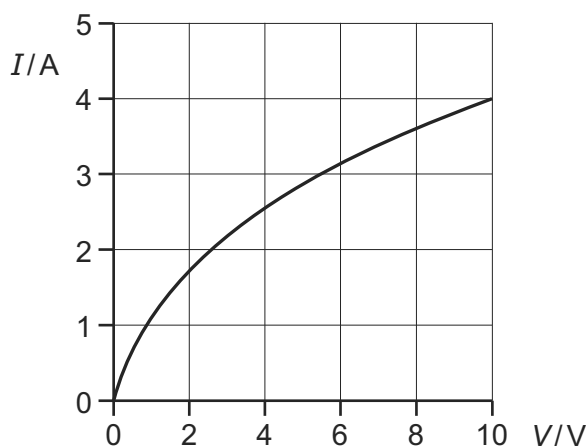


Since the graph is not a straight line, the resistance of the lamp varies with  $V$





Which row gives the correct resistance at the stated value of  $V$ ?

	$V/V$	$R/\Omega$
A	2.0	1.5
B	4.0	3.2
C	6.0	1.9
D	8.0	0.9




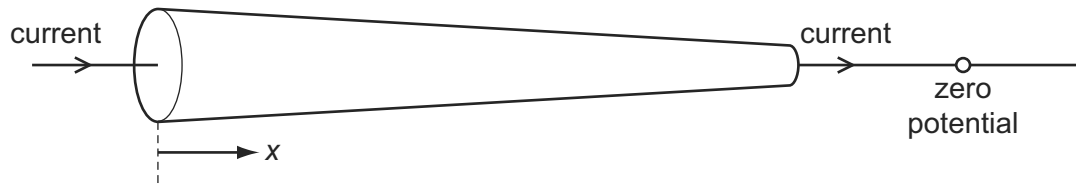
- 41** The circular cross-sectional area of a metal wire varies along its length. There is a current in the wire. The narrow end of the wire is at a reference potential of zero. 9702/13/M/J/13



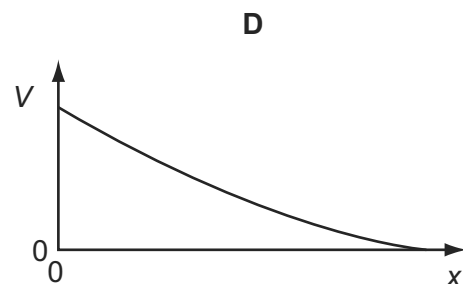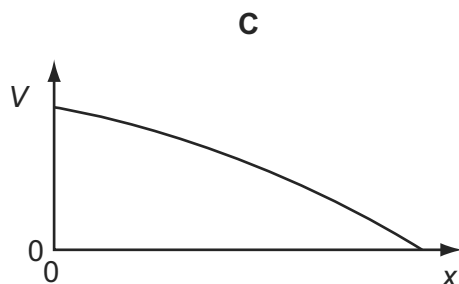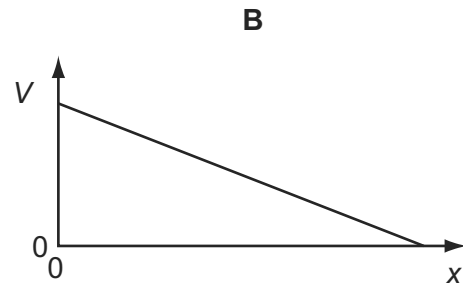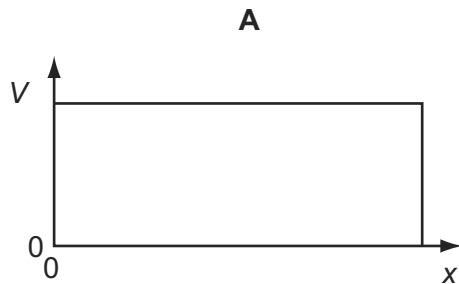Which graph best represents the variation with distance  $x$  along the wire of the potential difference  $V$  relative to the reference zero?



- 42** Which graph best represents the way the current  $I$  through a filament lamp varies with the potential difference  $V$  across it?

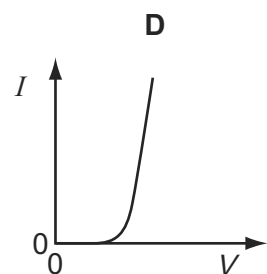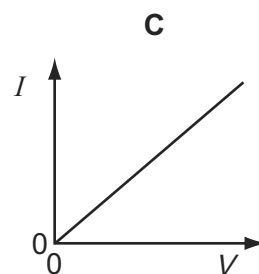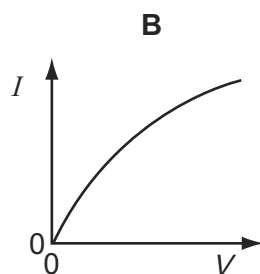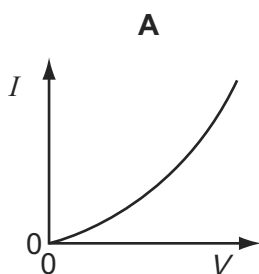[illegible]